



**higher education  
& training**

---

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

**T770(E)(J29)T**

**NATIONAL CERTIFICATE**

**INDUSTRIAL ELECTRONICS N3**

**(8080613)**

**29 July 2019 (X-Paper)**

**09:00–12:00**

**Calculators may be used.**

**This question paper consists of 8 pages and 1 formula sheet.**

**DEPARTMENT OF HIGHER EDUCATION AND TRAINING**  
**REPUBLIC OF SOUTH AFRICA**  
NATIONAL CERTIFICATE  
INDUSTRIAL ELECTRONICS N3  
TIME: 3 HOURS  
MARKS: 100

---

**INSTRUCTIONS AND INFORMATION**

1. Answer ALL the questions.
  2. Read ALL the questions carefully.
  3. Number the answers according to the numbering system used in this question paper.
  4. ALL calculations must be shown.
  5. ALL the final answers must be approximated accurately to THREE decimal places.
  6. Subsections of questions must be kept together.
  7. Use  $\pi = 3,142$
  8. Write neatly and legibly.
-

**SECTION A****QUESTION 1**

1.1 Indicate whether the following statements are TRUE or FALSE. Choose the answer and write only 'True' or 'False' next to the question number (1.1.1–1.1.10) in the ANSWER BOOK.

- 1.1.1 Kirchoff's second law states that the currents entering a point are equal to the current leaving that point. 
- 1.1.2 In a capacitive circuit, current leads the voltage by 90°.
- 1.1.3 Resonance takes place in an RL circuit.
- 1.1.4  The nucleus of an atom consists of electrons and protons.
- 1.1.5 Avalanche breakdown applies to Zener diodes.
- 1.1.6 In an NPN transistor the holes are the majority charge carriers.
- 1.1.7 Cyclotronic control is a combination of the phase and the cycle control methods.
- 1.1.8 Intrinsic materials are sometimes referred to as pure materials.
- 1.1.9 A Zener diode conducts in both directions.
- 1.1.10 Sensitivity in measuring instruments refers to the time taken by the meter to provide a reading. 

(10 × 1) (10)

1.2 Choose a description from COLUMN B that matches an item in COLUMN A. Write only the letter (A–J) next to the question number (1.2.1–1.2.10) in the ANSWER BOOK.

| COLUMN A |                           | COLUMN B |                      |
|----------|---------------------------|----------|----------------------|
| 1.2.1    | Push-pull amplifier       | A        | forced commutation   |
| 1.2.2    | Seven-segment display     | B        | magnetic field       |
| 1.2.3    | Clipper                   | C        | digital voltmeter    |
| 1.2.4    | Piezo-electric transducer | D        | dynamic impedance    |
| 1.2.5    | Continuous balance        | E        | cathode-ray tube     |
| 1.2.6    | SCR                       | F        | 741 DIL              |
| 1.2.7    | Parallel RLC circuit      | G        | light-emitting diode |
| 1.2.8    | Operational amplifier     | H        | ultrasonic cleaning  |
| 1.2.9    | Oscilloscope              | I        | class AB             |
| 1.2.10   | Inductor                  | J        | PN diode             |

(10)  
[20]

TOTAL SECTION A: 20

SECTION B

QUESTION 2

Study FIGURE 1 and calculate the voltage as well as the power across resistor  $R_1$  by using Kirchhoff's laws.

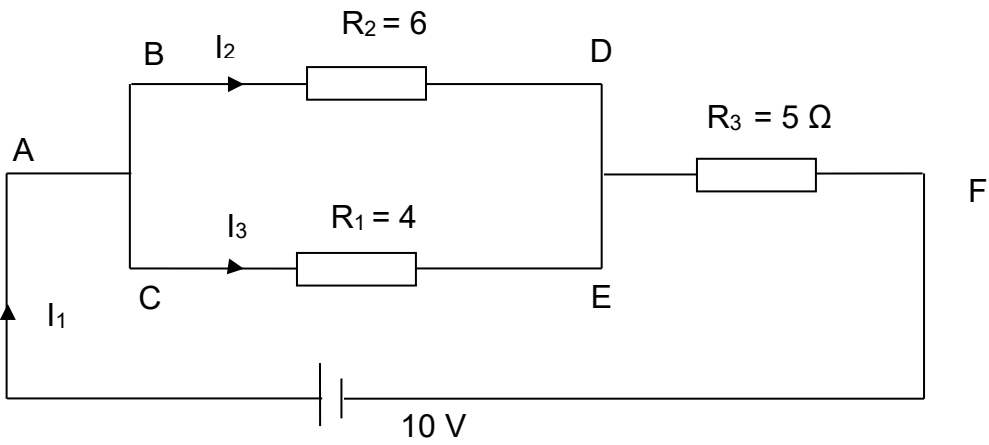
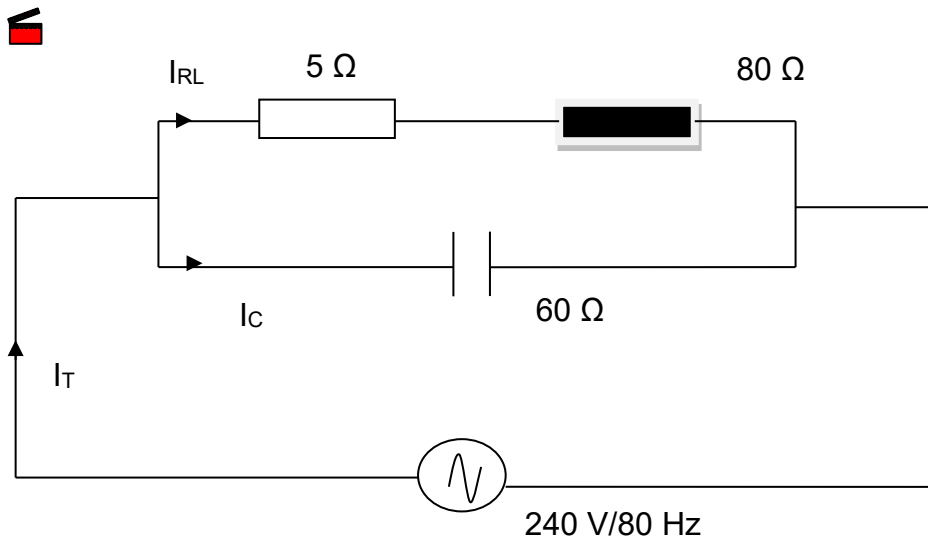


FIGURE 1

[14]

**QUESTION 3**

3.1 Refer to the circuit in FIGURE 2 and do the following calculations:

**FIGURE 2**

3.1.1 The current  $I_{RL}$  (3)

3.1.2 The current  $I_C$  (2)

3.1.3 The phase angle  $\theta_L$  of the inductive branch (2)

3.2 If the circuit in FIGURE 2 is considered to be at resonance, calculate the following from the circuit:

3.2.1 The dynamic impedance (4)

3.2.2 The total current in the circuit (2)

3.2.3 The value of the current  $I_C$  at resonance (2)

**[15]**

**QUESTION 4**

- 4.1 Draw a neat, labelled circuit of a half-wave voltage doubler. (5)
- 4.2 Briefly describe the operation of the circuit in QUESTION 4.1 when a positive signal is applied to the input.  (3)
- 4.3 Draw a neat, labelled characteristic curve of a varactor diode. (3)
- [11]**

**QUESTION 5**

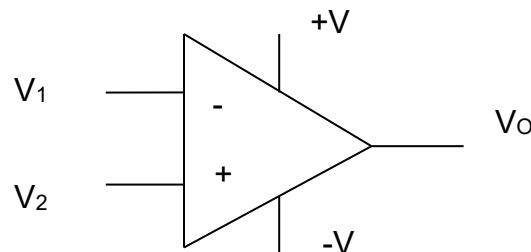
- 5.1 State FOUR advantages of using a transistor as a switch instead of a conventional switch.  (4)
- 5.2 Draw a neat, labelled frequency response graph of an RC coupling circuit. (4)
- [8]**

**QUESTION 6**

- 6.1 Draw a neat, labelled circuit diagram of an SCR by using transistors only. (4)
- 6.2  Briefly describe how the circuit mentioned in QUESTION 6.1 operates when a positive signal is applied on the gate terminal. (4)
- 6.3 State THREE advantages of an SCR. (3)
- [11]**

**QUESTION 7**

- 7.1 Indicate whether the following statements are TRUE or FALSE. Choose the answer and write only 'True' or 'False' next to the question number (7.1.1–7.1.3) in the ANSWER BOOK.


**FIGURE 3**

- 7.1.1 In FIGURE 3, if  $V_1 > V_2$  then  $V_0$  will be positive. (3)
- 7.1.2 In FIGURE 3, if  $V_1 < V_2$  then  $V_0$  will be negative. (3)
- 7.1.3 The operational amplifier can also be called a differential amplifier. (3 × 1) (3)
- 7.2 Draw a neat, labelled circuit diagram of an LVDT inductive transducer. (4)
- 7.3 Describe the operation of the circuit mentioned in QUESTION 7.2, if a force is applied to the core of the circuit. (4)

**[11]**

**QUESTION 8**

- 8.1 Refer to the block diagram of the oscilloscope shown in FIGURE 4 and name the parts labelled in the diagram, by writing only the answer next to the letter (a–i) in the ANSWER BOOK.

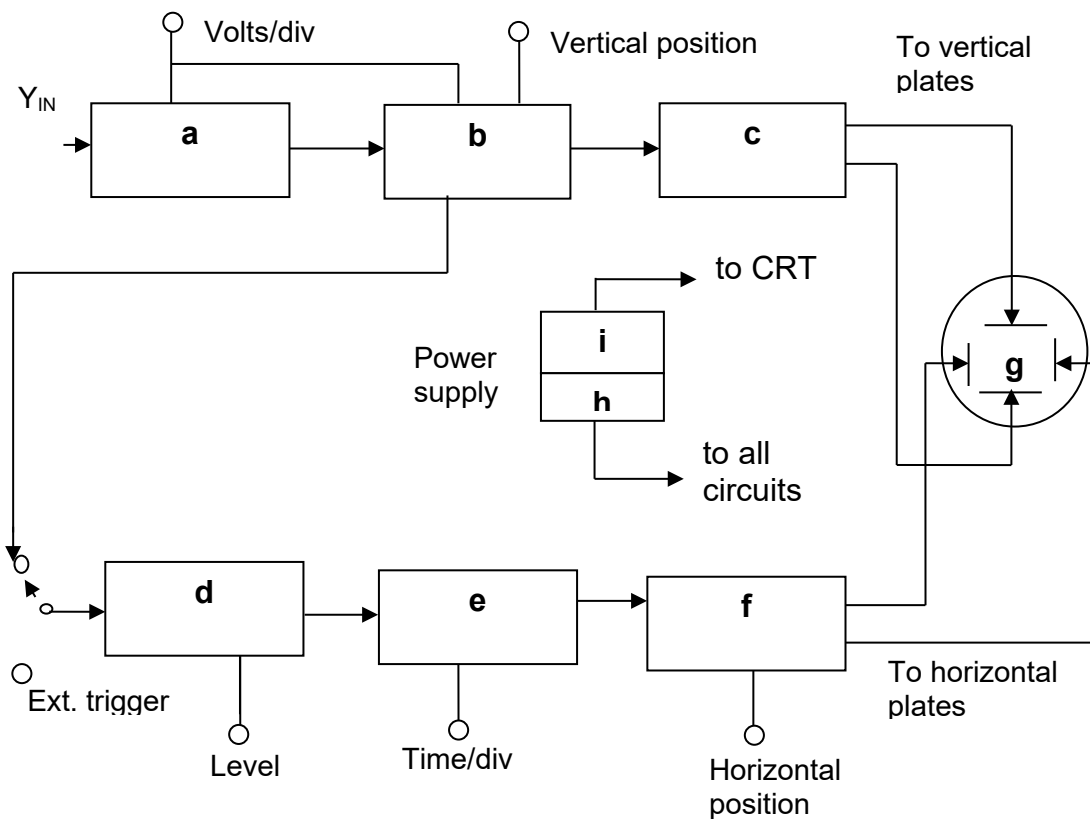**FIGURE 4**

(9)

- 8.2 Describe the function of the part named (a) in FIGURE 4.

(1)  
[10]

**TOTAL SECTION B: 80**  
**GRAND TOTAL: 100**

## INDUSTRIAL ELECTRONICS N3

### FORMULA SHEET

#### *Direct-current theory*

$$V = I \cdot R$$
$$P = V \cdot I$$
$$P = I^2 \cdot R$$
$$P = \frac{V^2}{R}$$

#### *Alternating-current theory*

$$X_L = 2\pi fL$$
$$X_C = \frac{1}{2\pi fC}$$
$$Z = \sqrt{R^2 + (X_L \sim X_C)^2}$$

$$V_T = \sqrt{V_R^2 + (V_L \sim V_C)^2}$$
$$I = \frac{V_T}{Z}$$
$$\theta = \cos^{-1} \frac{R}{Z}$$

$$V = I \cdot R$$
$$V = I \cdot X_L$$
$$V = I \cdot X_C$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$
$$I_R = \frac{V_T}{R}$$
$$I_L = \frac{V_T}{X_L}$$

$$I_C = \frac{V_T}{X_C}$$
$$I_T = \sqrt{I_R^2 + I_X^2}$$
$$I_X = I_L \sim I_C$$

$$\theta = \tan^{-1} \frac{I_X}{I_R}$$
$$\theta = \cos^{-1} \frac{I_R}{I_T}$$
$$Z = \frac{V}{I_T}$$

$$Z_D = \frac{L}{RC}$$
$$I_T = \frac{V}{Z_D}$$
$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$I_C = I_{RL} \sin \theta_L$$
$$I_T = I_{RL} \cos \theta_L$$
$$I_T = \sqrt{I_{TH}^2 + I_{TV}^2}$$

#### *Transistors*

$$I_C = \frac{V_{CC}}{R_L}$$

#### *Transducers*

$$R = \frac{\rho \cdot l}{a}$$
$$C = \frac{k \cdot A \cdot E_o}{d}$$