

NATIONAL CERTIFICATE COMMUNICATION-ELECTRONICS N5

(8080235)

1 February 2022 (X-paper) 09:00–12:00

Drawing instruments and nonprogrammable calculators may be used.

This question paper consists of 6 pages and a formula sheet of 5 pages.

028Q1E2201

Copyright reserved Please turn over

(8080235) -2-

DEPARTMENT OF HIGHER EDUCATION AND TRAINING REPUBLIC OF SOUTH AFRICA

NATIONAL CERTIFICATE
COMMUNICATION-ELECTRONICS N5
TIME: 3 HOURS
MARKS: 100

INSTRUCTIONS AND INFORMATION

- Answer all the questions.
- 2. Read all the questions carefully.
- Number the answers according to the numbering system used in this question paper.
- 4. Sketches should be large and neat and may be done in pencil.
- 5. Only use a black or blue pen.
- 6. Write neatly and legibly.

Copyright reserved Please turn over

(8080235) -3-

QUESTION 1: AC NETWORKS

1.1 Refer to the circuit diagram in FIGURE 1 (below) and calculate the following if the Q-factor is 75:



- 1.1.2 The voltage across the inductor (3)
- 1.1.3 The voltage across the capacitor (2)
- 1.1.4 The capacitor value at resonance (3)
- 1.1.5 The resonance frequency

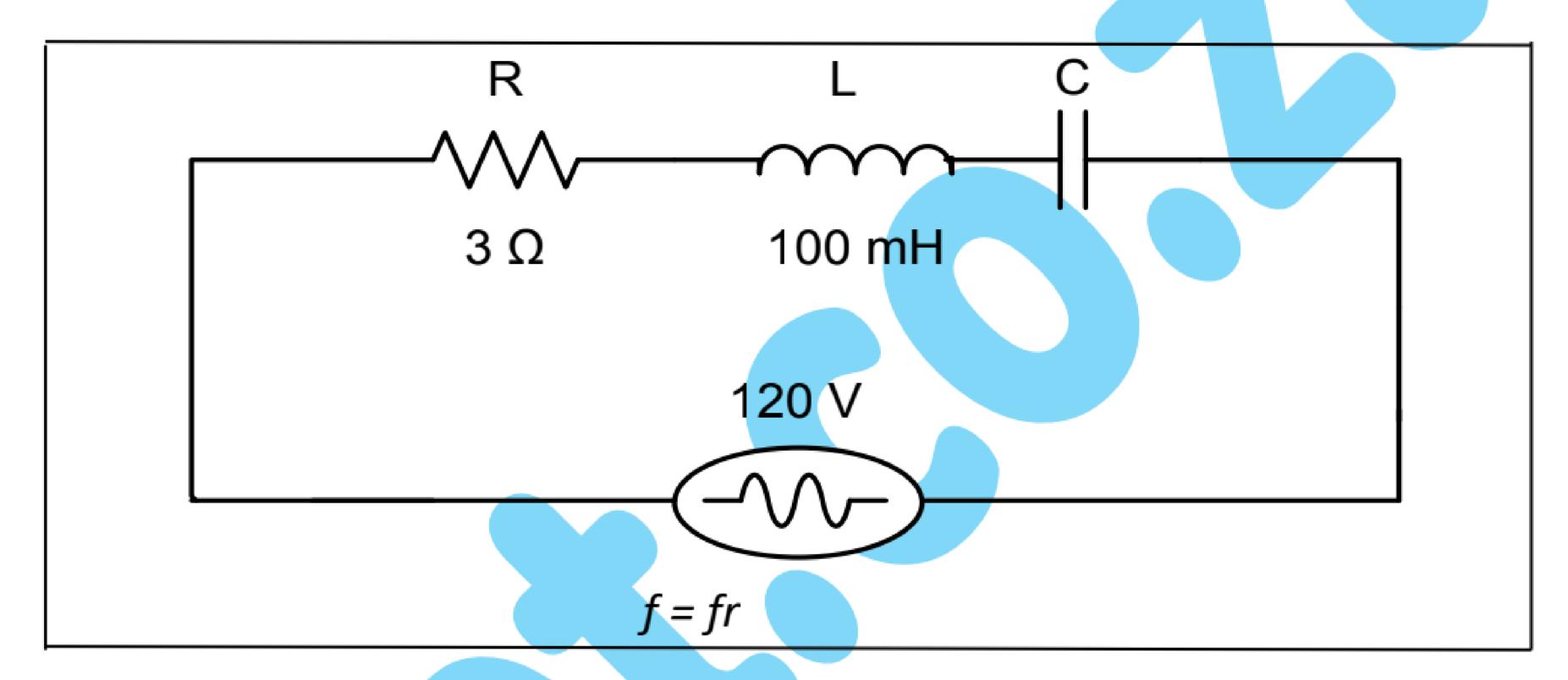


FIGURE 1

1.2 The dynamic impedance ZD = L/CR for a parallel resonant circuit.

1.3 Define mutual inductance. (2) [23]

QUESTION 2: TRUE OR FALSE

Indicate whether the following statements are TRUE or FALSE by writing only 'True' or 'False' next to the question number (2.1–2.10) in the ANSWER BOOK.

- In parallel resonance circuits, the current is maximum and the circuit is called a rejecter circuit.
- 2.2 A symmetrical two-port network has similar input and output ports that may not be interchanged.
- 2.3 An L-type attenuator is not normally used for matching purposes.
- In a low-pass filter circuit, all reactance-frequency curves slope upwards to the right and they have a positive slope.
- 2.5 Over-modulation in an AM transmitter has the effect of signal distortion.

Copyright reserved Please turn over