



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

NATIONAL CERTIFICATE

INDUSTRIAL ELECTRONICS N3

1 April 2020

This marking guideline consists of 12 pages.

SECTION A**QUESTION 1**

1.1	1.1.1	A	(5 × 1)	(5)
	1.1.2	B		
	1.1.3	D		
	1.1.4	B		
	1.1.5	C		
1.2	1.2.1	True	(5 × 1)	(5)
	1.2.2	True		
	1.2.3	False		
	1.2.4	True		
	1.2.5	False		
1.3	1.3.1	D	(5 × 1)	(5)
	1.3.2	B		
	1.3.3	E		
	1.3.4	A		
	1.3.5	F		
1.4	1.4.1	MOSFET	(5 × 1)	(5)
	1.4.2	Differentiator		
	1.4.3	Negative temperature coefficient		
	1.4.4	Leads		
	1.4.5	Forward biased		
				[20]

TOTAL SECTION A: 20

SECTION B**QUESTION 2**

2.1 2.1.1 In Loop ABEFA:

$$V = I_1.R_1 + (I_1 - I_2)R_L + I_1.R_4$$

$$48 = 15I_1 + 5(I_1 - I_2) + 18I_1$$

$$48 = 15I_1 + 5I_1 - 5I_2 + 18I_1$$

$$48 = 38I_1 - 5I_2 \quad \text{_____} \quad (1) \quad \checkmark \quad \checkmark$$

In Loop ABCDEFA:

$$V = I_1.R_1 + I_2.R_2 + I_2.R_3 + I_1.R_4$$

$$48 = 15I_1 + 10I_2 + 7I_2 + 18I_1$$

$$48 = 33I_1 + 17I_2 \quad \text{_____} \quad (2) \quad \checkmark \quad \checkmark$$

$$(1) \times 17$$

$$816 = 646I_1 - 85I_2 \quad \text{_____} \quad (3) \quad \checkmark$$

$$(2) \times 5$$

$$240 = 165I_1 + 85I_2 \quad \text{_____} \quad (4) \quad \checkmark$$

$$(3) + (4)$$

$$816 = 646I_1 - 85I_2$$

$$240 = 165I_1 + 85I_2$$

$$\hline 1056 = 811I_1$$

$$I_1 = \frac{1056}{811}$$

$$\underline{I_1 = 1,302 A} \quad \checkmark$$

$$48 = 38I_1 - 5I_2$$

$$48 = 38.(1,302) - 5I_2$$

$$-I_2 = \frac{48 - 49,476}{5}$$

$$\underline{I_2 = 0,295 A} \quad \checkmark$$

$$I_1 - I_2 = 1,302 - 0,295$$

$$\underline{I_1 - I_2 = 1,007 A} \quad \checkmark$$

(9)

$$\begin{aligned}
 2.1.2 \quad P &= (I_1 - I_2)^2 \times R_L \\
 P &= 1,007^2 \times 5 \quad \checkmark \\
 P &= 5,070W \quad \checkmark
 \end{aligned}
 \tag{2}$$

$$\begin{aligned}
 2.2 \quad 2.2.1 \quad X_L &= 2\pi \cdot f \cdot L \\
 X_L &= 2\pi \times 50 \times 25 \times 10^{-3} \quad \checkmark \\
 X_L &= 7,854\Omega \quad \checkmark \\
 \\
 X_C &= \frac{1}{2\pi \cdot f \cdot C} \\
 X_C &= \frac{1}{2\pi \times 50 \times 45 \times 10^{-6}} \quad \checkmark \\
 X_C &= 70,736\Omega \quad \checkmark \\
 \\
 Z &= \sqrt{R^2 + (X_C - X_L)^2} \\
 Z &= \sqrt{35^2 + (70,736 - 7,854)^2} \quad \checkmark \\
 Z &= 71,966\Omega \quad \checkmark
 \end{aligned}
 \tag{6}$$

$$\begin{aligned}
 2.2.2 \quad I &= \frac{V}{Z} \\
 I &= \frac{220}{71,966} \quad \checkmark \\
 I &= 3,057A \quad \checkmark
 \end{aligned}
 \tag{2}$$


$$\begin{aligned}
 2.2.3 \quad Z_{RL} &= \sqrt{R^2 + X_L^2} \\
 Z_{RL} &= \sqrt{35^2 + 7,854^2} \quad \checkmark \\
 Z_{RL} &= 35,870\Omega \quad \checkmark \\
 \\
 V_{RL} &= I \cdot Z_{RL} \\
 V_{RL} &= 3,057 \times 35,87 \quad \checkmark \\
 V_{RL} &= 109,655V \quad \checkmark
 \end{aligned}
 \tag{4}$$

$$\begin{aligned}
 2.2.4 \quad V_C &= I \cdot X_C \\
 V_C &= 3,057 \times 70,736 \quad \checkmark \\
 V_C &= 216,240V \quad \checkmark
 \end{aligned}
 \tag{2}$$

(2)
[25]


QUESTION 3

3.1 3.1.1

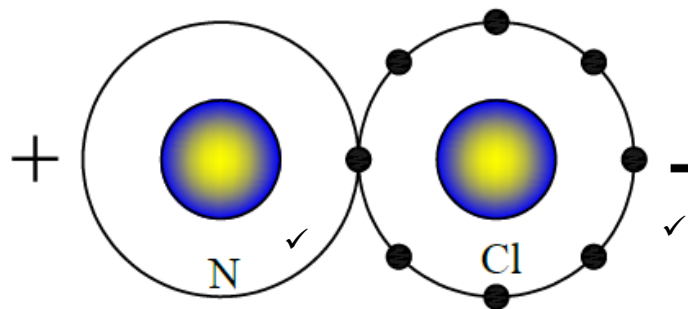


(2)

3.1.2

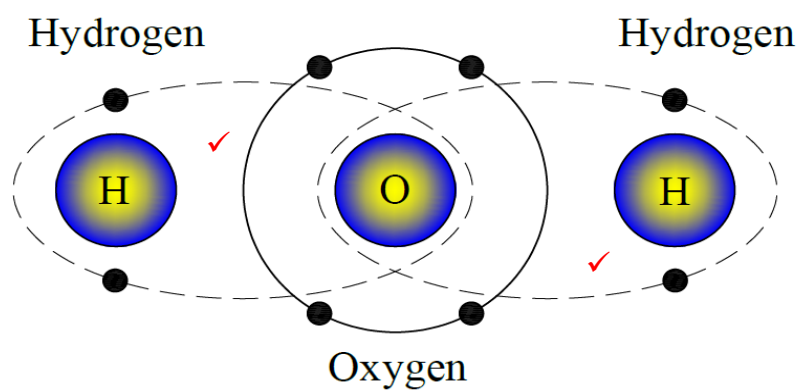

(2)


3.2 3.2.1

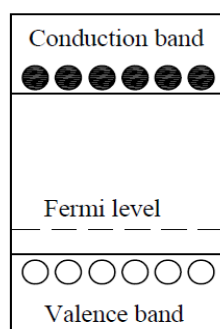

P-Type Material

(2)

3.2.2

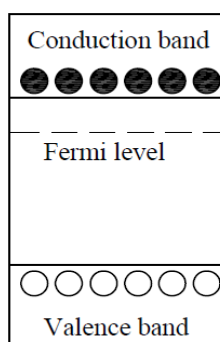


N-Type Material

(2)


3.3 3.3.1 Reverse current✓ flowing at specified Zener test current to provide nominal Zener voltage✓ (2)

3.3.2 Specified voltage✓ at a specific test current✓ (2)

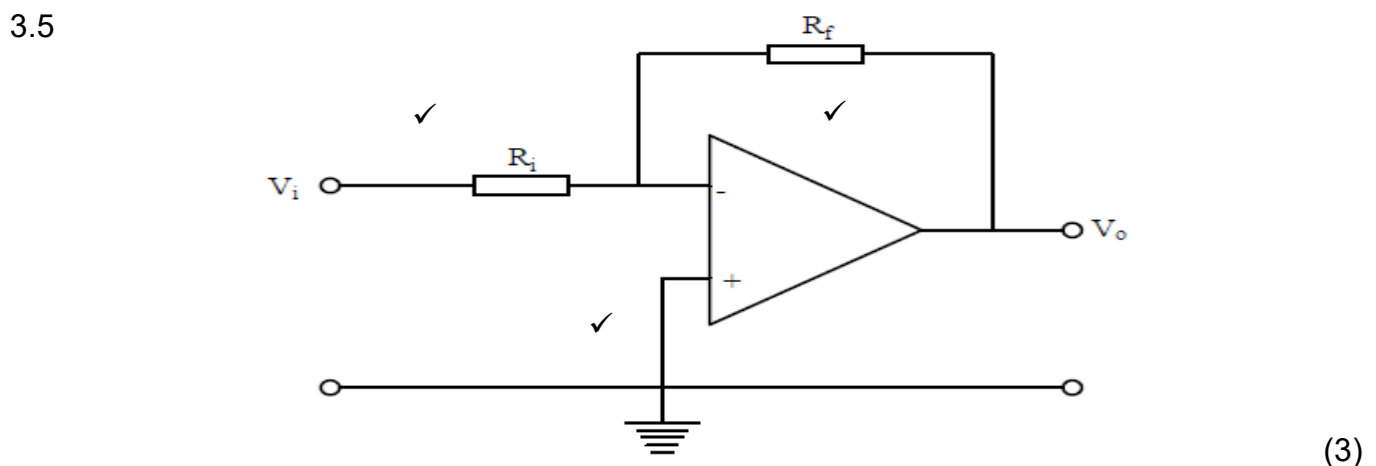3.4 When light falls on the PN-junction electron-hole pairs are created which increase the availability of minority carriers. The minority carrier under reverse-biased conditions causes an increase in leakage current.✓ As the light intensity increases the leakage current increases and the diode becomes more conductive.✓ (2)



3.6 Used for matching high impedance output to low impedance input (1)

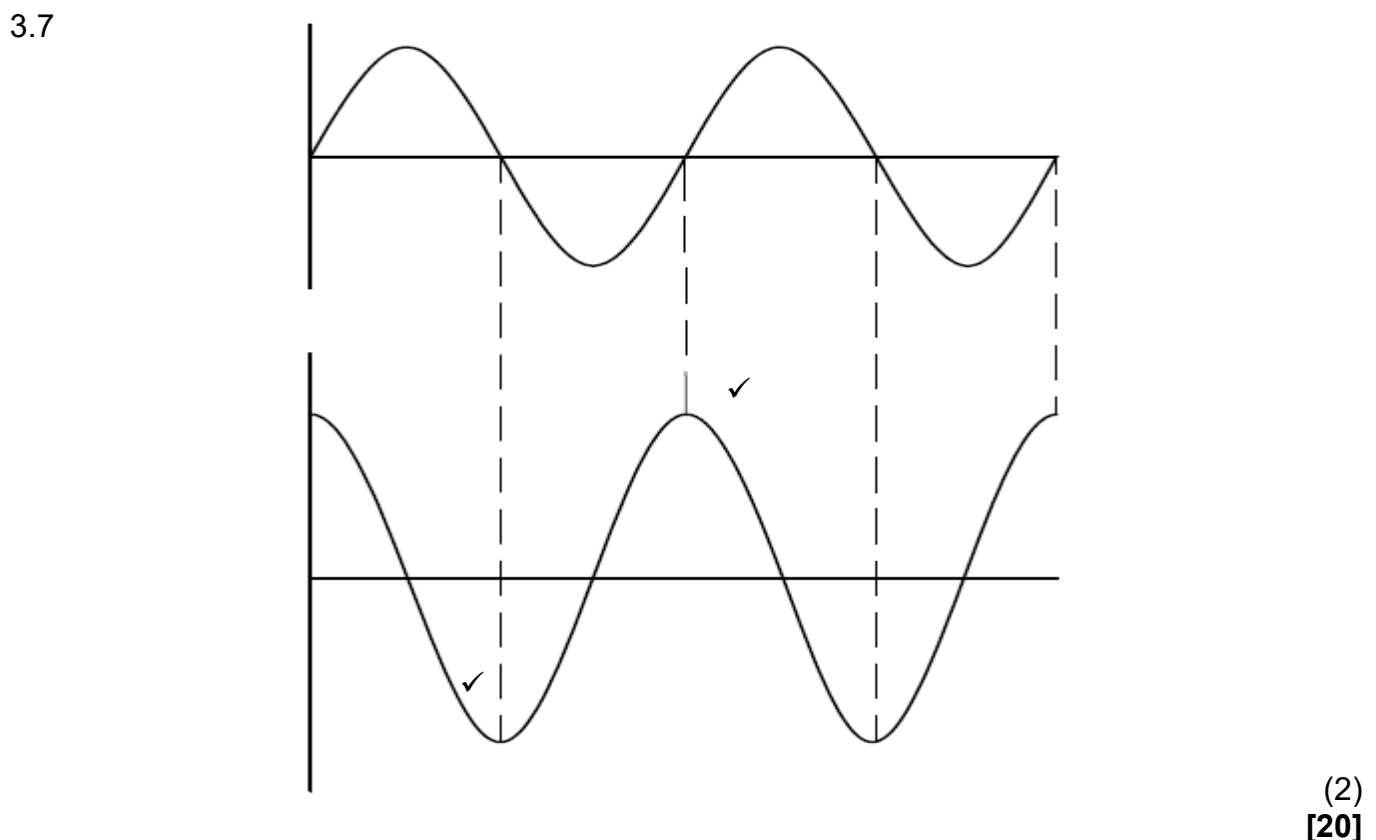

QUESTION 4

4.1 4.1.1


$$I_C = \frac{V_{CE}}{R_C}$$

$$I_C = \frac{12}{3 \times 10^3} \checkmark$$

$$\underline{\underline{I_C = 4mA \checkmark}}$$


(2)

4.1.2

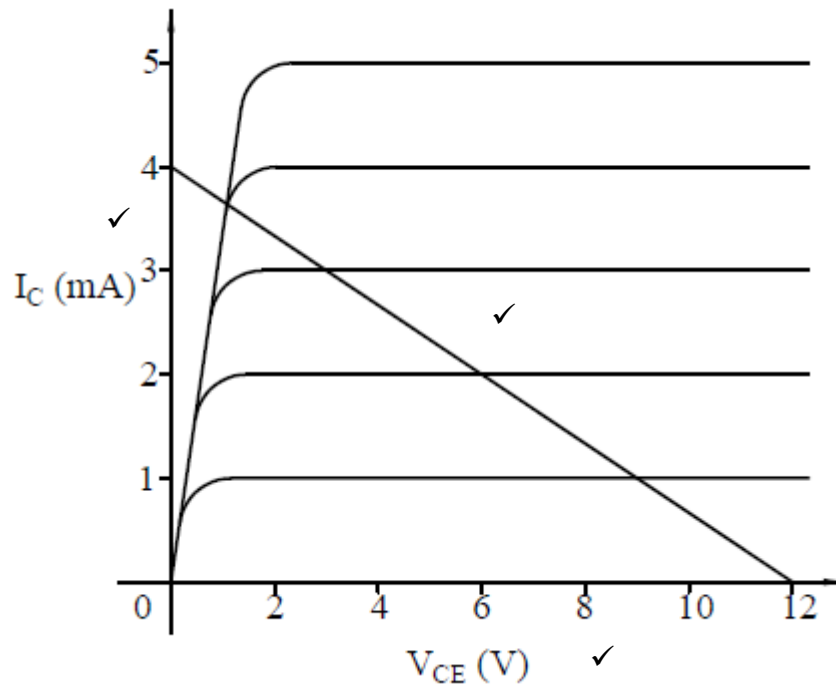


(2)

4.2

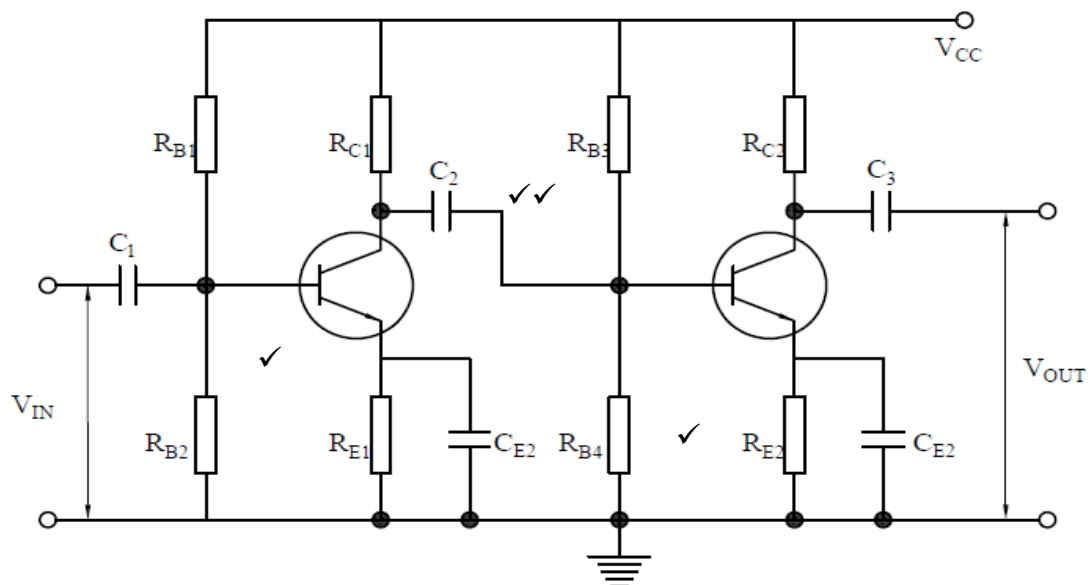


(4)

4.3 4.3.1

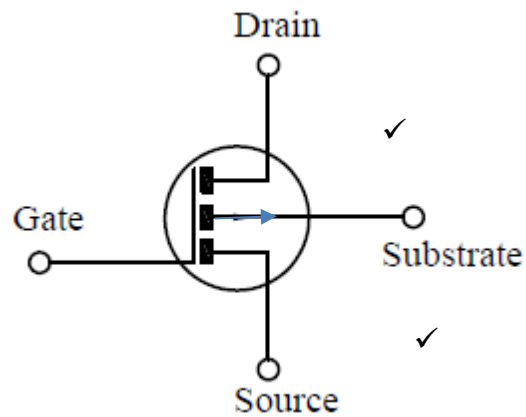


(2)

4.3.2

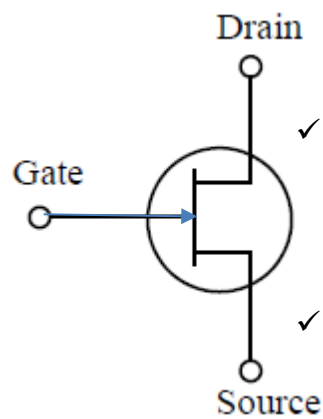


(2)

4.4

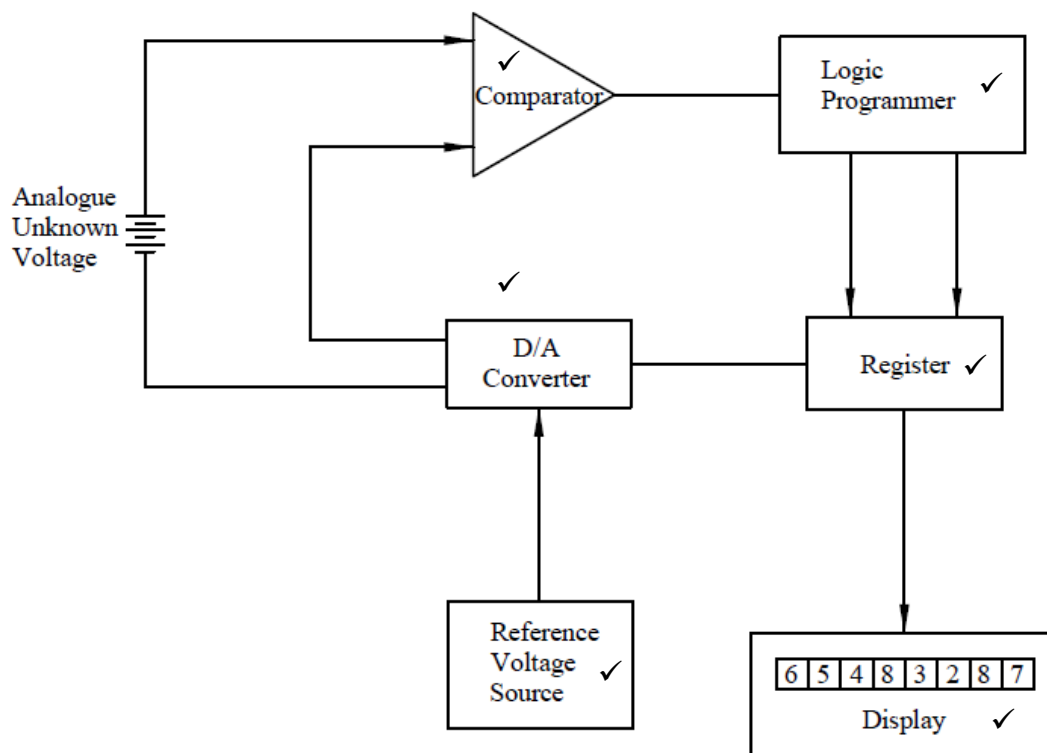

OR

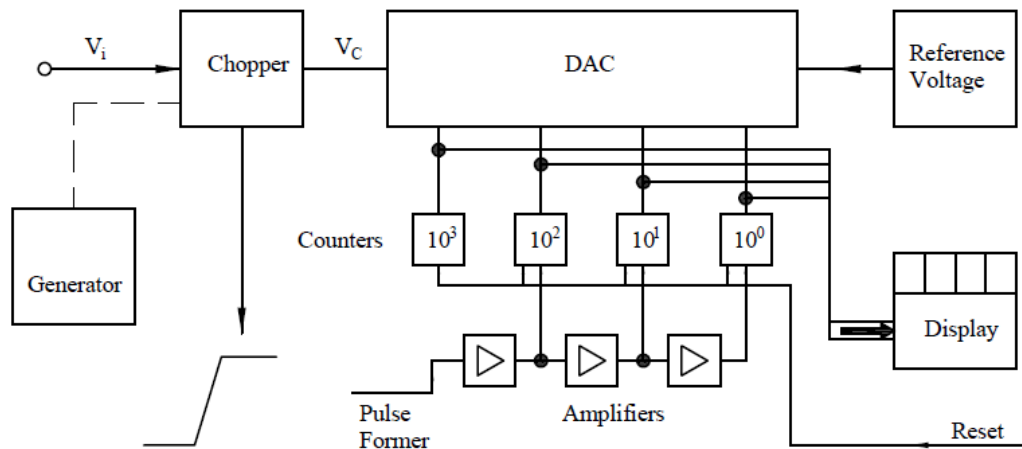

(6)

- 4.5 Deflection plates position the CRT spot✓ anywhere on the screen by simultaneous application of appropriate vertical and horizontal voltage inputs✓

(2)

[20]**QUESTION 5**

- 5.1 5.1.1 Moving the magnetic core by an externally applied force✓ varies the difference in voltage of the two secondary windings✓ of the transformer. The magnitude of this difference is an indication of the direction & magnitude of applied force.✓

(3)

- 5.1.2
- Pressure – force
 - Displacement – linear movement
 - Position – direction of movement

(Any 2 × 1)


(2)

- 5.2
- Sound – microphones, speakers
 - Acceleration – accelerometer
 - Pressure changes – force measuring
 - Vibration – ultrasonic cleaning

(Any 2 × 1)


(2)

5.3

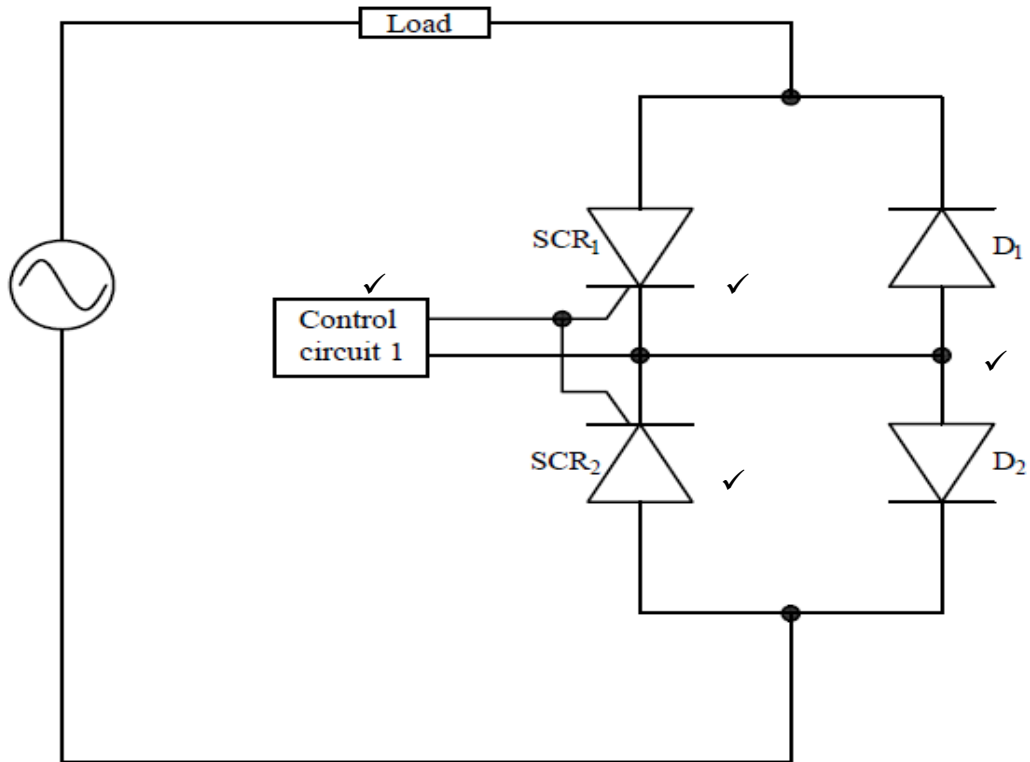

OR

(4)

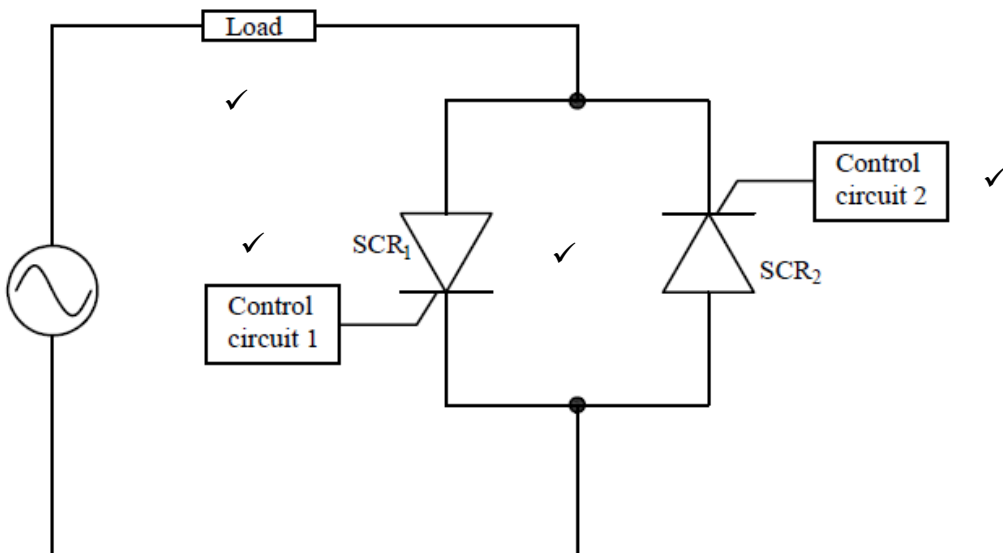

5.4 Voltage goes through zero and reduces the current below the holding current,
✓ forcing the SCR from conduction to OFF-state. ✓ (2)

5.5

- Line commutation
- Forced commutation

(2)
[15]

TOTAL SECTION B: 80
GRAND TOTAL: 100